

Karnaugh Maps (K-map)

- Alternate representation of a truth table
 - Red decimal = minterm value
 - Note that A is the MSB for this minterm numbering
 - Adjacent squares have distance = 1
- Valuable tool for logic minimization
- Applies most Boolean theorems & postulates automatically (when procedure is followed)

form 1

| | | | |
|--|--|---|---|
| $\begin{array}{c} B \\ \diagdown \\ A \end{array}$ | | 0 | 1 |
| | | 0 | 1 |
| | | 0 | 1 |
| | | 0 | 1 |

2-variable
K-Maps

form 2

| | | | |
|--|--|---|---|
| $\begin{array}{c} B \\ \diagdown \\ A \end{array}$ | | 0 | 1 |
| | | 0 | 1 |
| | | 0 | 1 |
| | | 0 | 1 |

Karnaugh Maps (K-map)

- Alternate forms of 3-variable K-maps

➤ Note end-around adjacency

- Distance = 1
- Note: A is MSB, C is LSB for minterm numbering

form 1

| | | BC | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| A | 0 | 01 | | | 32 |
| | 1 | 45 | | | 76 |

form 2

| | B | | | |
|---|---|----|--|----|
| | | | | |
| A | | 01 | | 32 |
| | | 45 | | 76 |

| AB | C | |
|----|----|----|
| | 0 | 1 |
| 00 | 01 | |
| 01 | 23 | |
| 11 | | 67 |
| 10 | | 45 |

| | C | | | |
|---|---|----|--|----|
| | | | | |
| A | | 01 | | 67 |
| | | 23 | | 45 |

K-mapping & Minimization Steps

Step 1: generate K-map

- Put a 1 in all specified minterms
- Put a 0 in all other boxes (optional)

Step 2: group all adjacent 1s without including any 0s

- All groups (aka *prime implicants*) must be rectangular and contain a “power-of-2” number of 1s
 - 1, 2, 4, 8, 16, 32, ...
- An essential group (aka *essential prime implicant*) contains at least 1 minterm not included in any other groups
 - A given minterm may be included in multiple groups

Step 3: define product terms using variables common to all minterms in group

Step 4: sum all essential groups plus a minimal set of remaining groups to obtain a minimum SOP

K-map Minimization Example


- $Z = \sum_{A,B,C}(1,3,6,7)$

➤ Recall SOP minterm implementation

- 8 gates
 - 27 gate I/O
- K-map results
- 4 gates
 - 11 gate I/O

| BC A | | BC | | | |
|---------|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 4 | 5 | 7 | 6 |
| | | 0 | 0 | 1 | 1 |

essential prime implicants

 

Note: this group not needed since 1s are already covered


| A | B | C | Z | Row value |
|---|---|---|---|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 2 |
| 0 | 1 | 1 | 1 | 3 |
| 1 | 0 | 0 | 0 | 4 |
| 1 | 0 | 1 | 0 | 5 |
| 1 | 1 | 0 | 1 | 6 |
| 1 | 1 | 1 | 1 | 7 |

K-map Minimization Goals

- Larger groups:
 - Smaller product terms
 - Fewer variables in common
 - Smaller AND gates
 - In terms of number of inputs
- Fewer groups:
 - Fewer product terms
 - Fewer AND gates
 - Smaller OR gate
 - ✓ In terms of number of inputs
 - Invert output
 - Use NOR instead of OR gate
- Alternate method:
 - Group 0s
 - Could produce fewer and/or smaller product terms

4-variable K-maps

 - Note adjacency of 4 corners as well as sides
- Variable ordering for this minterm numbering: ABCD



5-variable K-map

- Note adjacency between maps when overlaid
 - distance=1
- Variable order for this minterm numbering:
 - A,B,C,D,E (A is MSB, E is LSB)

| BC \ DE | | A=0 | | | |
|---------|----|-------|----|-------|-----|
| | | 00 | 01 | 11 | 10 |
| BC | 00 | 0 1 | | | 3 2 |
| | 01 | 4 5 | | | 7 6 |
| | 11 | 12 13 | | 15 14 | |
| | 10 | 8 9 | | 11 10 | |

| BC \ DE | | A=1 | | | |
|---------|----|-------|----|-------|----|
| | | 00 | 01 | 11 | 10 |
| BC | 00 | 16 17 | | 19 18 | |
| | 01 | 20 21 | | 23 22 | |
| | 11 | 28 29 | | 31 30 | |
| | 10 | 24 25 | | 27 26 | |

5-variable K-map

- Changing the variable used to separate maps changes minterm numbering
- Same variable order for this minterm numbering:
 - A,B,C,D,E (A is MSB, E is LSB)

| AB \ CD | | E=0 | | | |
|---------|----|-----|-------|----|-------|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | | 0 2 | | 6 4 |
| | 01 | | 8 10 | | 14 12 |
| | 11 | | 24 26 | | 30 28 |
| | 10 | | 16 18 | | 22 20 |

| AB \ CD | | E=1 | | | |
|---------|----|-----|-------|----|-------|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | | 1 3 | | 7 5 |
| | 01 | | 9 11 | | 15 13 |
| | 11 | | 25 27 | | 31 29 |
| | 10 | | 17 19 | | 23 21 |

6-variable K-map

- Variable order for minterm numbers: ABCDEF

A=0

| CD \ EF | 00 | 01 | 11 | 10 |
|---------|------|----|------|----|
| 00 | 01 | | 32 | |
| 01 | 45 | | 76 | |
| 11 | 1213 | | 1514 | |
| 10 | 89 | | 1110 | |

A=1

| CD \ EF | 00 | 01 | 11 | 10 |
|---------|------|----|------|----|
| 00 | 3233 | | 3534 | |
| 01 | 3637 | | 3938 | |
| 11 | 4445 | | 4746 | |
| 10 | 4041 | | 4342 | |

B=0

| CD \ EF | 00 | 01 | 11 | 10 |
|---------|------|------|----|----|
| 00 | 1617 | 1918 | | |
| 01 | 2021 | 2322 | | |
| 11 | 2829 | 3130 | | |
| 10 | 2425 | 2726 | | |

B=1

| CD \ EF | 00 | 01 | 11 | 10 |
|---------|------|------|----|----|
| 00 | 4849 | 5150 | | |
| 01 | 5253 | 5554 | | |
| 11 | 6061 | 6362 | | |
| 10 | 5657 | 5958 | | |

Don't Care Conditions

- Sometimes input combinations are of no concern
 - Because they may not exist
 - Example: BCD uses only 10 of possible 16 input combinations
 - Since we “don't care” what the output, we can use these “don't care” conditions for logic minimization
 - The output for a don't care condition can be either 0 or 1
 - ✓ WE DON'T CARE!!!
- Don't Care conditions denoted by:
 - X, -, d, 2
 - X is probably the most often used
- Can also be used to denote inputs
 - Example: $ABC = 1X1 = AC$
 - B can be a 0 or a 1

Don't Care Conditions

- Truth Table

- K-map

- Minterm


$$\triangleright Z = \Sigma_{A,B,C}(1,3,6,7) + d(2)$$

- Maxterm

$$\triangleright Z = \Pi_{A,B,C}(0,4,5) + d(2)$$

- Notice Don't Cares are same for both minterm & maxterm

$$Z = B + A'C$$

 

Circuit analysis:

$$G=3 \quad G_{IO}=8$$


(compared to $G=4$ & $G_{IO}=11$ w/o don't care)

| A | B | C | Z |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | X |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

| BC \ A | 00 | 01 | 11 | 10 |
|--------|----|------|----|------|
| 0 | 0 | 1 | 1 | X |
| 1 | 0 | 45 0 | 1 | 76 1 |


Design Example

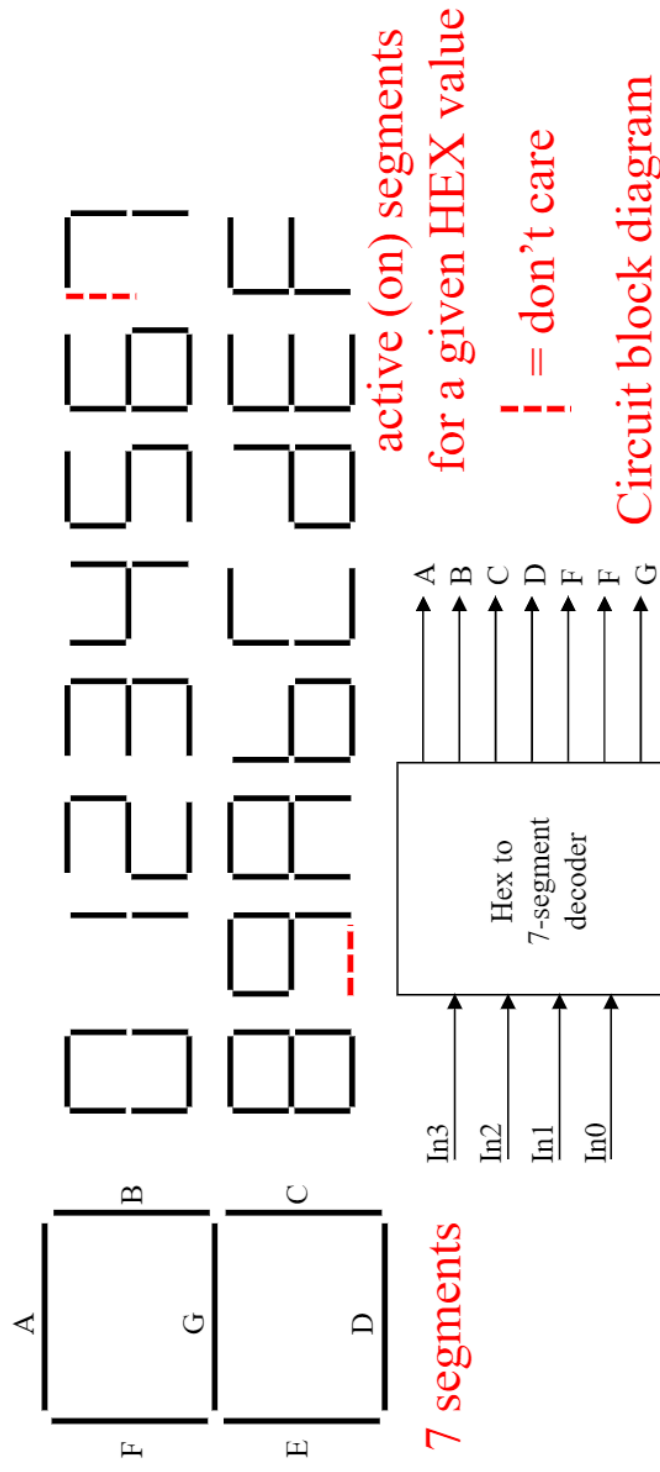- Hexadecimal to 7-segment display decoder
 - A common circuit in calculators
 - 7-segments (A-G) to represent digits (0-9 & A-F)
 - A logic 1 turns on given segment



HEX to 7-seg Design Example

- Create truth table from specification

 


| In3 | In2 | In1 | In0 | A | B | C | D | E | F | G |
|-----|-----|-----|-----|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | X | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | X | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |


HEX to 7-seg Design Example

- Generate K-maps & obtain logic equations

| In3 | In2 | In1 | In0 | A | B | C | D | E | F | G |
|-----|-----|-----|-----|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |

 




 
$$A = \text{In2}'\text{In0}' + \text{In3}'\text{In1} + \text{In2 In1} + \text{In3 In0}' + \text{In3}'\text{In2 In0} + \text{In3 In2}'\text{In1}'$$



$$B = \text{In2}'\text{In0}' + \text{In2}'\text{In1}' + \text{In3}'\text{In1}'\text{In0}' + \text{In3 In1}'\text{In0} + \text{In3}'\text{In1 In0}$$

HEX to 7-seg Design Example

    - K-maps & logic equations for outputs C-G



$$C = \text{In3 In2}' + \text{In1}'\text{In0} + \text{In2}'\text{In1}' + \text{In3}'\text{In0} + \text{In3}'\text{In2}$$


$$D = \text{In3}'\text{In2}'\text{In0}' + \text{In2}'\text{In1 In0} + \text{In2 In1}'\text{In0}$$

$$+ \text{In3 In1}' + \text{In2 In1 In0}'$$

$$E = \text{In2}'\text{In0}' + \text{In3 In2} + \text{In1 In0}' + \text{In3 In1}$$

$$F = \text{In1}'\text{In0}' + \text{In3 In2}' + \text{In2 In0}' + \text{In3 In1} + \text{In3}'\text{In2}$$
 
$$G = \text{In3 In2}' + \text{In1 In0}' + \text{In3 In0} + \text{In3}'\text{In2 In1}' + \text{In2}'\text{In1}$$




HEX to 7-seg Design Example

- Remaining steps to complete design:
 - Draw logic diagram (sharing common gates)
 - Analyze for optimization metrics: G , G_{IO} , G_{del} , P_{del}
 - ✓ See next page for logic diagram & circuit analysis
 - Simulate circuit for design verification
 - Debug & fix problems when output is incorrect
 - ✓ Check truth table against K-map population
 - ✓ Check K-map groups against logic equation product terms
 - ✓ Check logic equations against schematic
 - Optimize circuit for area and/or performance
 - Use Boolean postulates & theorems
 - Re-simulate & verify optimized design

loads
on PIs

HEX to 7-seg Design Example

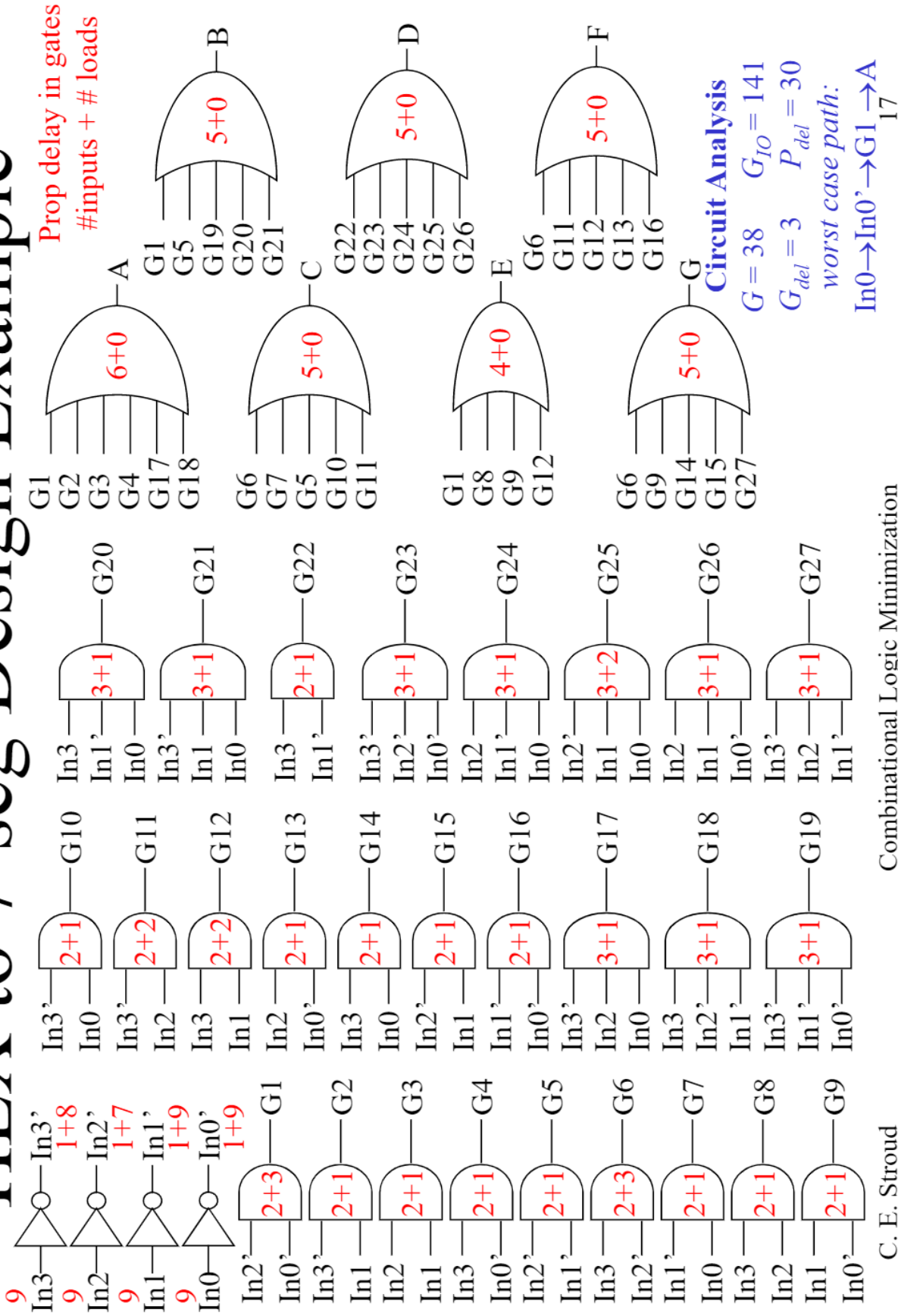

Combinational Logic Minimization
(9/12)

C. E. Stroud